## ELECTRICAL MEASUREMENTS.

in the circuit through the box of coils, when the resistance  $r_b$  is unplugged, it appears that

 $\frac{P}{p} = \frac{r_b + \rho_r}{r_b}$ 

But, according to § 192, and since the same condenser is used for both readings (*i.e.*, K=K')

 $\frac{P}{b} = \frac{D}{D'}$ 

Hence

$$\rho_{x} = \left\{ \frac{D}{D'} - \mathbf{1} \right\} r_{b}$$

whence  $\rho_x$  can be found. In practice  $r_b$  can generally be so adjusted as to make

D=2D'

In this case, therefore

$$\rho_x = r_b$$

This method will give good results, and is applicable to inconstant batteries; but it requires careful manipulation. Great care should be taken to prevent the leads connected to the box of coils from influencing the galvanometer.

## MEASUREMENT OF DIFFERENCE OF POTENTIAL.

**224.** The general problem is to measure the difference of potential between any two points in a circuit. Let these two points be denoted by A and B; let  $p_a$  be the potential at A, and  $p_b$  that at B, then  $p_a - p_b$  is the difference of potential between A and B.

These measurements are made by comparing  $p_a - p_b$  with some known difference of potential, such as that furnished by a standard cell.

225. The cells to be used, to obtain the known difference of potential, are either Latimer Clark's standard, Grove's, Bunsen's, or Daniell's.\*

## BY LAW'S CONDENSER METHOD.

**226.** One plate of the condenser is connected to the point  $B,\dagger$  and the other through a key to the point A; a reflecting galvanometer is introduced between A and the condenser, as shown in

\*See §§ 158-161.

†See § 224.

132