

News, New Inventions, Scientific Achievements, In the World of Radio

RADIO RECEIVING SETS

Continued From Last Week.

By W. B. Cartmel, B.S., M.A., M.E.I.C., Northern Electric Company Limited, Montreal
ARTICLE VI.

In the last few years very radical changes have been made in receiving sets. Our magazines have been filled with all sorts of different hook-ups. These all belong to the three classes of receiving sets previously mentioned, by far the larger part belonging to the regenerative class. It is not surprising that the regenerative hook-up should have attracted so much attention when we remember what tremendous distances one may obtain reception by this method using only a single tube. Radio-frequency hook-ups, however, are coming more to the front at the present time because people are becoming more critical in their requirements, and radio-frequency not only gives reception from distances greater, even than may be reached by means of regeneration, but will more important, being the distant stations in much more greatly and clear. A new type of hook-up is now coming into use

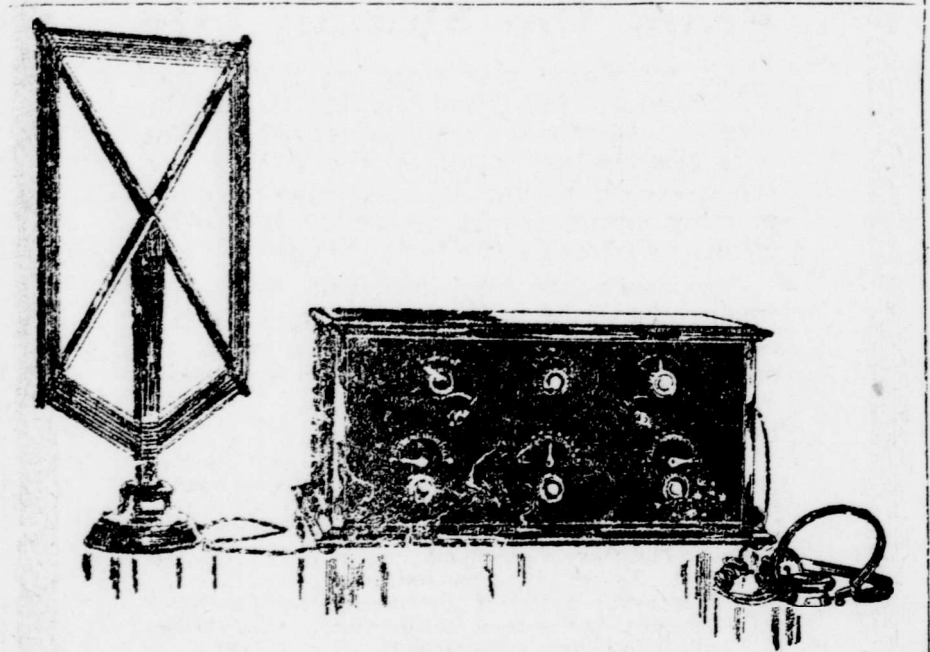


FIG. 1.

which has much very remarkable qualities that at the best of existing radio-technique I feel compelled to describe a superior to it. This set is shown in figure 1, expected to a small loop antenna, and figure 2 gives an interior view of the set. It will be noted that there are six vacuum tubes used, which are necessary in order to produce the remarkable results that may be obtained from a set of this kind. The operation, however, is not as costly as it might seem, because the total amount of B battery consumed by the six tubes is less than would be required for a single one of the larger tubes. The whole super-heterodyne need not

be between tubes just as we do in the case of audio-frequency, whereas air core transformers only are used in amplifying at short wavelengths. More important than this, the vacuum tube itself does not amplify as efficiently at short wavelengths as it does at long wavelengths in fact, at very short wavelengths it amplifies very badly indeed. Not only that, but very curiously the vacuum tube produces even higher amplification at these long wavelengths than at audio-frequencies. At audio-frequency we obtain an amplification from 250 to 250 times. At short wave radio-frequency the amplification per

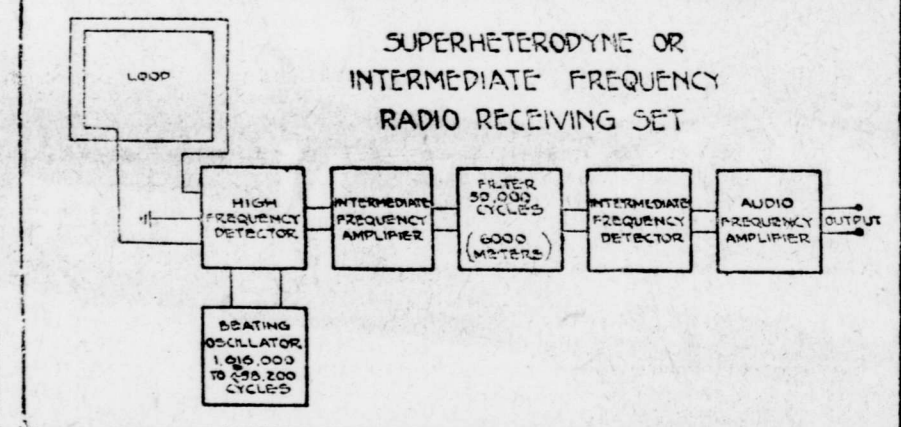


FIG. 3.

stage is less than this, while the radio-frequency amplification in some super-heterodynes is as much as 5,000 times per stage. This will give us some idea of the tremendous amplification given by one or two stages of intermediate frequency amplification. With such tremendous amplification previous to detection, a very weak signal indeed may be brought up to sufficient strength to permit of detection, especially when we remember how weak a signal may be detected by a vacuum tube.

Perhaps we can understand best about the operation of a super-heterodyne by considering figure 3, in which the super-heterodyne is shown divided up into its different elements. At the left we see that there is a loop antenna which

are detected. It will be readily understood that a set of this kind requires the utmost skill and experience in order to be made up in such a way as to give the best results. When made up properly, however, such a set leaves nothing to be desired as regards simplicity of operation and the purity which it will bring in the reproduction of musical notes as transmitted by radio. On the other hand, if a set of this kind is made up without giving due regard to all of the finer details of design, the results produced will be very poor, just as the quality of received music is concerned, although it is not so difficult to make a super-heterodyne that will give marvellously long-distance reception merely on a loop.

RADIO NOTES.

Get a good grade of porcelain insulator for your aerial.

Yale has started a "communications course."

There are 36 broadcasters in Canada. Rubber tape is better than friction tape for aerial work.

There are 3,000 radio manufacturers and 1,000 distributors and jobbers in the United States.

Three of the world's most powerful transmitting stations are in Moscow. French amateur has been heard from Paris to Algeria with a two-tube receiver on 25 meters.

Station KPNF, Suenandach, Pa., has a pig for mascot.

Rub panel with pumice on long distance reception.

Grid and plate leads of tube sockets should be away from the panel.

About 100 German firms are manufacturing amateur radio apparatus and parts.

United States navy is gradually substituting tube sets for the old-fashioned spark.

Station KGO, Oakland, Calif., reports an orphanage of Eskimo children at Teller, Alaska, among its fans. Variometer shafts should be of brass or copper, not of iron or steel.

Once the reception is good, let the set alone.

King George of England has a seven-tube receiving set.

Simultaneous broadcasting in England has received great popularity.

A broadcast receiving license in Great Britain costs \$2.50 a year.

British amateurs recently heard an Argentine station.

China technically bans radio under an embargo forbidding the importation of anything usable as war material.

For economy buy a honeycomb coil, rather than make one.

Wilson was the first United States president to broadcast his voice.

Sunlight shortens the life of a storage battery.

Acid should not be used as a soldering flux, because it attacks the copper.

Radio manufacturers and others suggest the use of "radioact" instead of "broadcast."

American Radio Relay League is building up amateur radio stations in foreign countries.

RADIO REVIEW

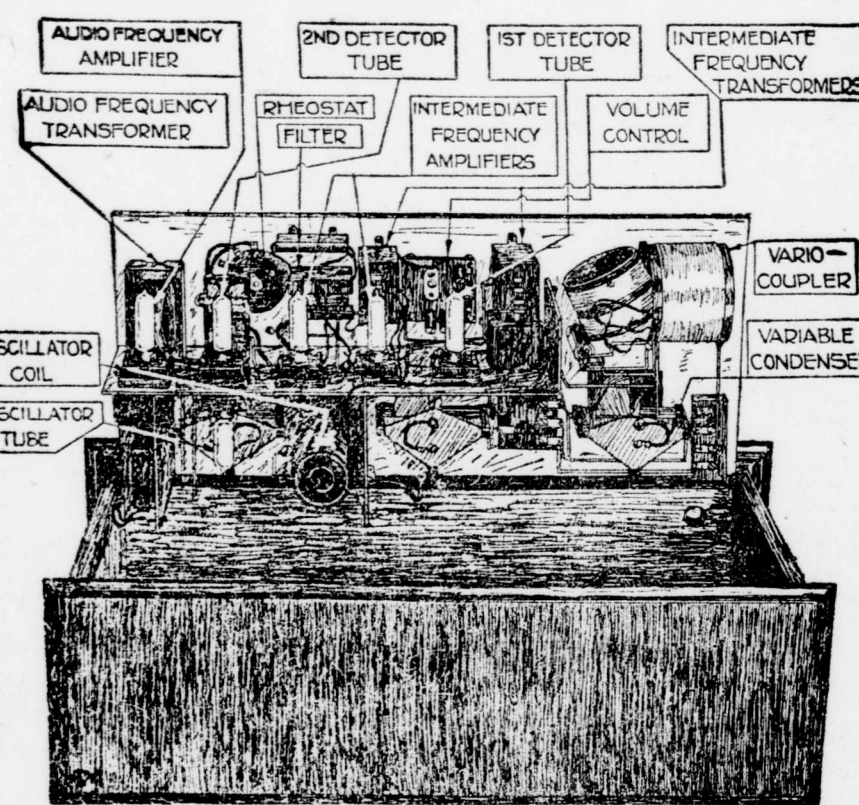


FIG. 2.

SUPERHETERODYNE RECEIVER

brings the incoming signals to the high frequency detector. It will be noted that there is an oscillator connected to the high-frequency detector, furnishing high-frequency vibrations which combine with those received by the loop, giving them a lower frequency or longer wavelength than they had when received by the loop. In the first high-frequency detector the wavelength is changed to exactly 5,000 meters, or in other words a vibration frequency of 50,000 vibrations per second. No matter what the wavelength of the incoming waves, they are always changed to exactly this wavelength and this wavelength only. Following the high-frequency detector is the intermediate frequency amplifier. There are two stages of intermediate frequency amplification, two tubes and two transformers being shown for this purpose in figure 2. After having been given these two stages of amplification at a wavelength of 5,000 meters, the signals are passed through a filter which clarifies them and eliminates noises. This filter consists of an coil wound on a wooden spool and a condenser, the two being shown together as indicated by a two-headed arrow in figure 2. After leaving the filter the signals are detected and made audible by the second detector and then after detection are again amplified at audio-frequency.

Although this may seem like a complicated method of receiving radio signals, we may explain the whole thing simply by saying that the signals are changed from short wavelength signals to long wavelength signals so that they are more easily amplified, and then after being amplified twice they

bring the incoming signals to the high frequency detector. It will be noted that there is an oscillator connected to the high-frequency detector, furnishing high-frequency vibrations which combine with those received by the loop, giving them a lower frequency or longer wavelength than they had when received by the loop. In the first high-frequency detector the wavelength is changed to exactly 5,000 meters, or in other words a vibration frequency of 50,000 vibrations per second. No matter what the wavelength of the incoming waves, they are always changed to exactly this wavelength and this wavelength only. Following the high-frequency detector is the intermediate frequency amplifier. There are two stages of intermediate frequency amplification, two tubes and two transformers being shown for this purpose in figure 2. After having been given these two stages of amplification at a wavelength of 5,000 meters, the signals are passed through a filter which clarifies them and eliminates noises. This filter consists of an coil wound on a wooden spool and a condenser, the two being shown together as indicated by a two-headed arrow in figure 2. After leaving the filter the signals are detected and made audible by the second detector and then after detection are again amplified at audio-frequency.

Although this may seem like a complicated method of receiving radio signals, we may explain the whole thing simply by saying that the signals are changed from short wavelength signals to long wavelength signals so that they are more easily amplified, and then after being amplified twice they

bring the incoming signals to the high frequency detector. It will be noted that there is an oscillator connected to the high-frequency detector, furnishing high-frequency vibrations which combine with those received by the loop, giving them a lower frequency or longer wavelength than they had when received by the loop. In the first high-frequency detector the wavelength is changed to exactly 5,000 meters, or in other words a vibration frequency of 50,000 vibrations per second. No matter what the wavelength of the incoming waves, they are always changed to exactly this wavelength and this wavelength only. Following the high-frequency detector is the intermediate frequency amplifier. There are two stages of intermediate frequency amplification, two tubes and two transformers being shown for this purpose in figure 2. After having been given these two stages of amplification at a wavelength of 5,000 meters, the signals are passed through a filter which clarifies them and eliminates noises. This filter consists of an coil wound on a wooden spool and a condenser, the two being shown together as indicated by a two-headed arrow in figure 2. After leaving the filter the signals are detected and made audible by the second detector and then after detection are again amplified at audio-frequency.

Although this may seem like a complicated method of receiving radio signals, we may explain the whole thing simply by saying that the signals are changed from short wavelength signals to long wavelength signals so that they are more easily amplified, and then after being amplified twice they

bring the incoming signals to the high frequency detector. It will be noted that there is an oscillator connected to the high-frequency detector, furnishing high-frequency vibrations which combine with those received by the loop, giving them a lower frequency or longer wavelength than they had when received by the loop. In the first high-frequency detector the wavelength is changed to exactly 5,000 meters, or in other words a vibration frequency of 50,000 vibrations per second. No matter what the wavelength of the incoming waves, they are always changed to exactly this wavelength and this wavelength only. Following the high-frequency detector is the intermediate frequency amplifier. There are two stages of intermediate frequency amplification, two tubes and two transformers being shown for this purpose in figure 2. After having been given these two stages of amplification at a wavelength of 5,000 meters, the signals are passed through a filter which clarifies them and eliminates noises. This filter consists of an coil wound on a wooden spool and a condenser, the two being shown together as indicated by a two-headed arrow in figure 2. After leaving the filter the signals are detected and made audible by the second detector and then after detection are again amplified at audio-frequency.

Although this may seem like a complicated method of receiving radio signals, we may explain the whole thing simply by saying that the signals are changed from short wavelength signals to long wavelength signals so that they are more easily amplified, and then after being amplified twice they

bring the incoming signals to the high frequency detector. It will be noted that there is an oscillator connected to the high-frequency detector, furnishing high-frequency vibrations which combine with those received by the loop, giving them a lower frequency or longer wavelength than they had when received by the loop. In the first high-frequency detector the wavelength is changed to exactly 5,000 meters, or in other words a vibration frequency of 50,000 vibrations per second. No matter what the wavelength of the incoming waves, they are always changed to exactly this wavelength and this wavelength only. Following the high-frequency detector is the intermediate frequency amplifier. There are two stages of intermediate frequency amplification, two tubes and two transformers being shown for this purpose in figure 2. After having been given these two stages of amplification at a wavelength of 5,000 meters, the signals are passed through a filter which clarifies them and eliminates noises. This filter consists of an coil wound on a wooden spool and a condenser, the two being shown together as indicated by a two-headed arrow in figure 2. After leaving the filter the signals are detected and made audible by the second detector and then after detection are again amplified at audio-frequency.

Although this may seem like a complicated method of receiving radio signals, we may explain the whole thing simply by saying that the signals are changed from short wavelength signals to long wavelength signals so that they are more easily amplified, and then after being amplified twice they

bring the incoming signals to the high frequency detector. It will be noted that there is an oscillator connected to the high-frequency detector, furnishing high-frequency vibrations which combine with those received by the loop, giving them a lower frequency or longer wavelength than they had when received by the loop. In the first high-frequency detector the wavelength is changed to exactly 5,000 meters, or in other words a vibration frequency of 50,000 vibrations per second. No matter what the wavelength of the incoming waves, they are always changed to exactly this wavelength and this wavelength only. Following the high-frequency detector is the intermediate frequency amplifier. There are two stages of intermediate frequency amplification, two tubes and two transformers being shown for this purpose in figure 2. After having been given these two stages of amplification at a wavelength of 5,000 meters, the signals are passed through a filter which clarifies them and eliminates noises. This filter consists of an coil wound on a wooden spool and a condenser, the two being shown together as indicated by a two-headed arrow in figure 2. After leaving the filter the signals are detected and made audible by the second detector and then after detection are again amplified at audio-frequency.

Although this may seem like a complicated method of receiving radio signals, we may explain the whole thing simply by saying that the signals are changed from short wavelength signals to long wavelength signals so that they are more easily amplified, and then after being amplified twice they

bring the incoming signals to the high frequency detector. It will be noted that there is an oscillator connected to the high-frequency detector, furnishing high-frequency vibrations which combine with those received by the loop, giving them a lower frequency or longer wavelength than they had when received by the loop. In the first high-frequency detector the wavelength is changed to exactly 5,000 meters, or in other words a vibration frequency of 50,000 vibrations per second. No matter what the wavelength of the incoming waves, they are always changed to exactly this wavelength and this wavelength only. Following the high-frequency detector is the intermediate frequency amplifier. There are two stages of intermediate frequency amplification, two tubes and two transformers being shown for this purpose in figure 2. After having been given these two stages of amplification at a wavelength of 5,000 meters, the signals are passed through a filter which clarifies them and eliminates noises. This filter consists of an coil wound on a wooden spool and a condenser, the two being shown together as indicated by a two-headed arrow in figure 2. After leaving the filter the signals are detected and made audible by the second detector and then after detection are again amplified at audio-frequency.

Although this may seem like a complicated method of receiving radio signals, we may explain the whole thing simply by saying that the signals are changed from short wavelength signals to long wavelength signals so that they are more easily amplified, and then after being amplified twice they

bring the incoming signals to the high frequency detector. It will be noted that there is an oscillator connected to the high-frequency detector, furnishing high-frequency vibrations which combine with those received by the loop, giving them a lower frequency or longer wavelength than they had when received by the loop. In the first high-frequency detector the wavelength is changed to exactly 5,000 meters, or in other words a vibration frequency of 50,000 vibrations per second. No matter what the wavelength of the incoming waves, they are always changed to exactly this wavelength and this wavelength only. Following the high-frequency detector is the intermediate frequency amplifier. There are two stages of intermediate frequency amplification, two tubes and two transformers being shown for this purpose in figure 2. After having been given these two stages of amplification at a wavelength of 5,000 meters, the signals are passed through a filter which clarifies them and eliminates noises. This filter consists of an coil wound on a wooden spool and a condenser, the two being shown together as indicated by a two-headed arrow in figure 2. After leaving the filter the signals are detected and made audible by the second detector and then after detection are again amplified at audio-frequency.

Although this may seem like a complicated method of receiving radio signals, we may explain the whole thing simply by saying that the signals are changed from short wavelength signals to long wavelength signals so that they are more easily amplified, and then after being amplified twice they


bring the incoming signals to the high frequency detector. It will be noted that there is an oscillator connected to the high-frequency detector, furnishing high-frequency vibrations which combine with those received by the loop, giving them a lower frequency or longer wavelength than they had when received by the loop. In the first high-frequency detector the wavelength is changed to exactly 5,000 meters, or in other words a vibration frequency of 50,000 vibrations per second. No matter what the wavelength of the incoming waves, they are always changed to exactly this wavelength and this wavelength only. Following the high-frequency detector is the intermediate frequency amplifier. There are two stages of intermediate frequency amplification, two tubes and two transformers being shown for this purpose in figure 2. After having been given these two stages of amplification at a wavelength of 5,000 meters, the signals are passed through a filter which clarifies them and eliminates noises. This filter consists of an coil wound on a wooden spool and a condenser, the two being shown together as indicated by a two-headed arrow in figure 2. After leaving the filter the signals are detected and made audible by the second detector and then after detection are again amplified at audio-frequency.

Although this may seem like a complicated method of receiving radio signals, we may explain the whole thing simply by saying that the signals are changed from short wavelength signals to long wavelength signals so that they are more easily amplified, and then after being amplified twice they

bring the incoming signals to the high frequency detector. It will be noted that there is an oscillator connected to the high-frequency detector, furnishing high-frequency vibrations which combine with those received by the loop, giving them a lower frequency or longer wavelength than they had when received by the loop. In the first high-frequency detector the wavelength is changed to exactly 5,000 meters, or in other words a vibration frequency of 50,000 vibrations per second. No matter what the wavelength of the incoming waves, they are always changed to exactly this wavelength and this wavelength only. Following the high-frequency detector is the intermediate frequency amplifier. There are two stages of intermediate frequency amplification, two tubes and two transformers being shown for this purpose in figure 2. After having been given these two stages of amplification at a wavelength of 5,000 meters, the signals are passed through a filter which clarifies them and eliminates noises. This filter consists of an coil wound on a wooden spool and a condenser, the two being shown together as indicated by a two-headed arrow in figure 2. After leaving the filter the signals are detected and made audible by the second detector and then after detection are again amplified at audio-frequency.

Although this may seem like a complicated method of receiving radio signals, we may explain the whole thing simply by saying that the signals are changed from short wavelength signals to long wavelength signals so that they are more easily amplified, and then after being amplified twice they

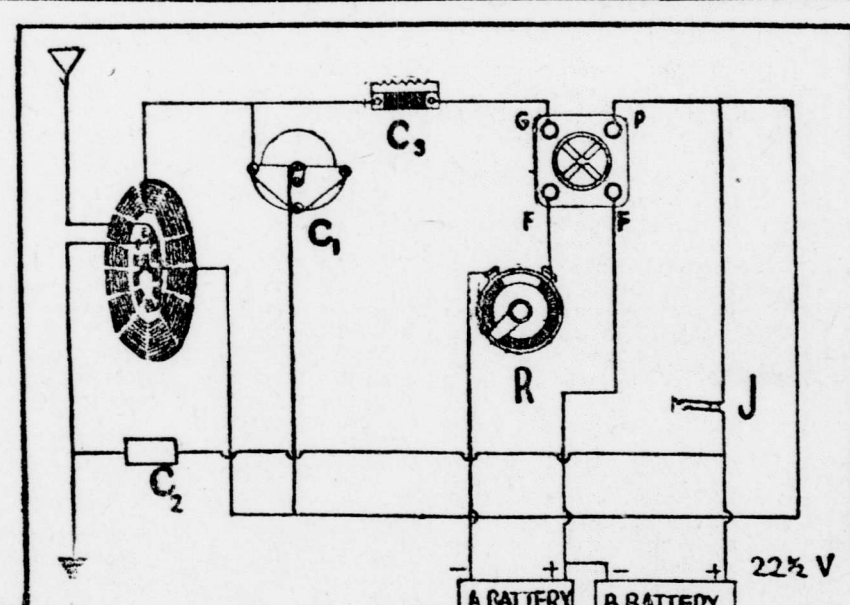LOW-LOSS COILS AND ONE CONTROL FOR DETECTOR



Hook-Up of One-Control Detector

BY ISRAEL KLEIN
Upon the low-loss coil depends much of the success in the construction of a simple detector. The tapped inductance, the variocoupler or variometer has given way to the honeycomb primary and secondary, the basket weave, diamond weave, spiderweb or similar type of winding. For it has been definitely established that there is a minimum of loss in reception by means of such coils.

A simple detector circuit with such coils has only one control, that of the variable condenser. Once the primary and secondary low-loss tuners are fixed, there is no longer need of tampering with them to tune in a station. The condenser does that.

A good type of coil for the set considered here is a simple spiderweb. Both the primary, A, and the secondary, B, are wound similarly around a two and a half inch inner circle. The best way to do this is to set an odd number of spikes, nine or 11 preferably, evenly around a thick wood hub, 2 1/2 inches in diameter, and wind the wire in and out about these, getting under two spikes over the next two, under the next two and so on.

CONDENSER IMPORTANT.
Coil A gets six windings of No. 16 DCC wire, while coil B is wound with about 48 turns of No. 18 wire. The exact number of windings depends on the condenser. Different condensers give varying results, therefore the best way to learn the exact number of turns needed is to experiment as follows:

Wind about 35 turns on the secondary, and when you are finished with the set and ready to listen, decide on a detector and tune in a station.

and was filtered through the sponge, allowing him to use the filtered static to recharge his batteries.

We are in receipt of a letter received from another fan, who states that he made use of A. Hick's suggestion with some success.

The writer states that he failed in his first attempt to catch static, owing to tuning in to a temperature station.

He says that the speech dried the sponge to a cinder.

His second attempt was also unsuccessful in that he tuned in to a speech being broadcast by advocates of Government control.

The sponge was saturated by the second speech, and in its soaking condition was of no use for filtering purposes.

The writer says his efforts were crowned with success in his third attempt when he tuned in to speeches being simultaneously broadcast by advocates of Government control and the O. T. A.

He states that the static from the "wet" speech just dripped down the funnel, and after filtering through the sponge was evaporized by the "dry" static.

Result was that at the end of the evening he had a pad full of concentrated static.

He placed this pad of static in the yard where he keeps his cows and one of the cows ate it, mistaking the substance for bran.

Now the writer declares that the cow that ate the plebeian static refuses to be milked unless a glassed rail, upon which it can rest one of its forefeet, is placed before it.

There are at least three wonderful things in this world: namely, radio, penitentiaries and laundries.

It is said that some laundrymen tear up shirts left over the weekend as an easy way to get rid of them.

Penitentiaries are full of men who have killed their laundrymen because the only washed part of their linen was the button-hole.

They at least got rid of the laundryman.

Both of the above have at least put the disappearing act on something.

Radio has its vituperative writers and critics, who, since the inception of radio, have endeavored to put the disappearing act on a few so-called artists.

Laundrymen are killed to save the trouble of looking for the shirtman because bearing a striking resemblance to penitentiaries and radio, in that they both save trouble in the family.

One night as I sat at my radio set I wuz weary an' ill at ease an' I twisted the dials idly 'tho' none of the tunes seemed to please. I don't know what stations I listened to or what I wuz dreaming when I heard the most wonderful music an' it brought back my youth again. I listened an' out of the stillness came those songs that we sang of old—"In the Evening" by the Moonlight, "Silver Threads Among

To-Day Is Your Last Opportunity To See Radio Show At Capitol Theater

TRADE WITH AMERICA IS CHIEF FACTOR IN JAPAN'S COMMERCE

TOKIO, Oct. 30.—Trade with the United States is still by far the leading factor in Japan's foreign commerce, according to figures for the empire's trade for the first half of 1924, issued by the department of finance. The United States bought 35.5 per cent. of Japan's exports during this period and

sold Japan 23.4 per cent. of her imports. America leads all countries in imports sold to Japan. Imports for the six months period totaled 1,462,000,000 yen, of which 432,000,000 yen represented purchases from the United States. India ranked second, with 270,000,000 yen, and Great Britain third, with 171,000,000 yen. Of the total exports, amounting to 805,000,000 yen, the United States bought 287,000,000 yen worth, China 194,000,000 yen, and France 45,000,000 yen.


"REGISTER" Your Name and Address

At our Booth in the "Radio Show" at the Capitol Theater. You may win a "Radio Set" free. Winner will be announced in Monday's Free Press.

RELIANCE GARAGE

RADIO DEALERS

J281

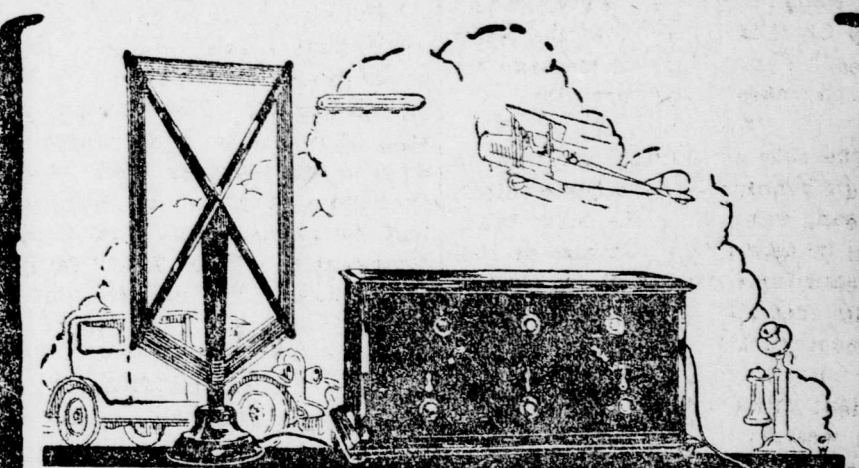

The Crowning Achievement of a Scientific Century

ALL that you have looked for in radio—the perfection your imagination has pictured—the absolute precision, the accuracy that enables you to "tune in" what you want—and "tune out" every thing else.

Best of all the marvellous clearness, modulation and richness of tones that give music its thrilling charm—

They are yours in this supreme achievement—

The Northern Electric R-4.

Cased in a handsome mahogany cabinet of genuine beauty and symmetry—a beautiful instrument—a set du Luxe.

To the radio expert R-4 is known as a 6-tube Super-Heterodyne Set. Patent Tubes give marvellous power and economy of operation. R-4 was used by the C.W. on the Prince of Wales train from New London to Alberta. Full information gladly sent on request.

Northern Electric COMPANY LIMITED

The people who made our "Phone"

HALIFAX	QUEBEC	OTTAWA	TORONTO
HAMILTON	LONDON	MONTREAL	WINDSOR
WINNIPEG	REGINA	CALGARY	VANCOUVER

Owners and Operators of
Broadcasting Station CHYC

Call at our store and hear the


W.M. Phillips
Northern Electric Radio Sets.
245 Dundas St. London
PHONE 1024.

We Are Dealers for Northern Electric Company's Products.

LONDON RADIO CO.

PHONE 2863. 298 DUNDAS STREET

McMURTRY HARDWARE, Limited

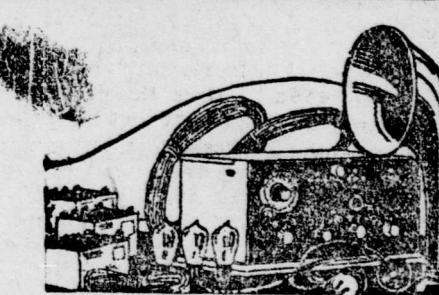ST. THOMAS, ONTARIO
Distributors for Northern Electric Products in Southwestern Ontario

You Will Become a Radio Enthusiast

If you once have one of our sets demonstrated for you. The long winter evenings are almost here. Have you made any preparations for entertainment? You will be able to sit in your own home and listen to music from far-off cities or a turn of the dial will bring lectures or concerts which are being broadcast closer to your own city.

DROP IN AND LET
US SHOW YOU

London Radio Shop

238 Dundas Street Phone 2863

Try this New RADIO TUBE

In your old set Ask your Dealer

Westinghouse

FOR SALE BY

Wm. Gurd & Co.
185 Dundas Street

FOR SALE BY

W.M. Phillips
238 Dundas St. London
PHONE 1026

RADIOLA

Simple to operate
Perfect in tone
Reasonable in price

Ask your dealer. Made by
CANADIAN WESTINGHOUSE COMPANY.
HAMILTON, ONTARIO

Westinghouse

CALL AT OUR STORE
AND HEAR WESTING.
HOUSE RADIOLAS.

W.M. Phillips
238 Dundas St. London

Westinghouse Radiola Sets

Sold and Installed by

WM. GURD & COMPANY
185 DUNDAS STREET - LONDON

Authorized representatives of

Westinghouse Radiolas

Gerhard Heintzman, Limited

322 DUNDAS STREET NEAR CLARENCE STREET

Full line always on hand.

Fascinating lectures



the father of Radio

Interesting talks on the swift-moving progress of science and the arts are sent into the air nightly from radio stations by world-famous authorities. As a means of keeping posted on the progress of mankind, radio is unequalled. For reception so clear that you seem to be in the room with the lecturer use a

MARCONIPHONE

Radio Receiver.

Write for descriptive booklet

THE MARCONI
WIRELESS TELEGRAPH CO. OF
CANADA LIMITED
MONTREAL



A FULL LINE OF

Marconi Radiophones

ALWAYS CARRIED BY

W.M. Phillips
238 Dundas St. London
PHONE 1026.

Your Radio Battery

Recharged for
50c

Called for and delivered,
\$1.00

Our Rechargeable "B" Batteries make a wonderful improvement on any set and we give, free, a Rectifier with a 48-Volt Battery.

Yours for better radio reception.</